

u3a Computing Group

Alan Hopwood, 7 March 2024

Agenda



Welcome

Current News, Issues and Questions

Topic Planning

Topic: integrated Circuit Design

AOB and Follow up

Presentation

Integrated Circuit Design

(Squeezing 2 University years into an hour)


Agenda

Integrated Circuit Design

- What are Integrated Circuits?
- Building Blocks
- Fabrication process

What are Integrated Circuits?

Integrated Circuit Design

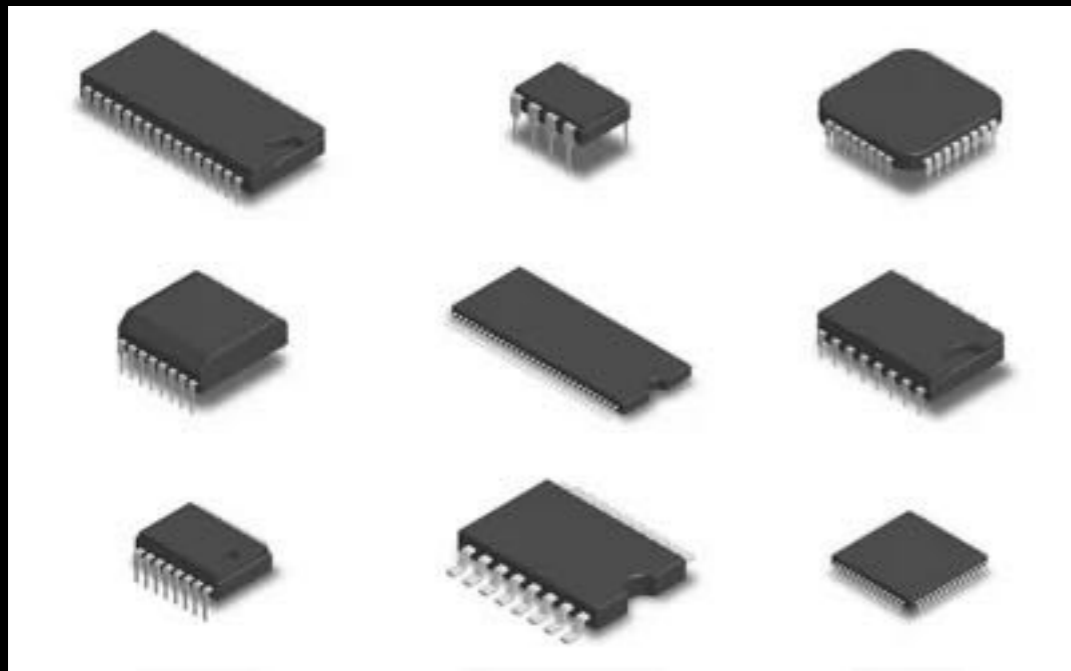

They are electronic devices made up of multiple interconnected electronic components such as transistors, resistors, and capacitors. These components are etched onto a small piece of semiconductor material, usually silicon.

Analogue ICs

- Power Supply chips
- Sensors
- Amplifiers
- RF applications
- Motor controllers
- ...


Digital ICs

- Memory (RAM, ROM, CMOS, Flash)
- Microprocessors
- Logic ICs
- Programmable ICs
- digital signal processors
- ...

What are Integrated Circuits


Integrated Circuit Design

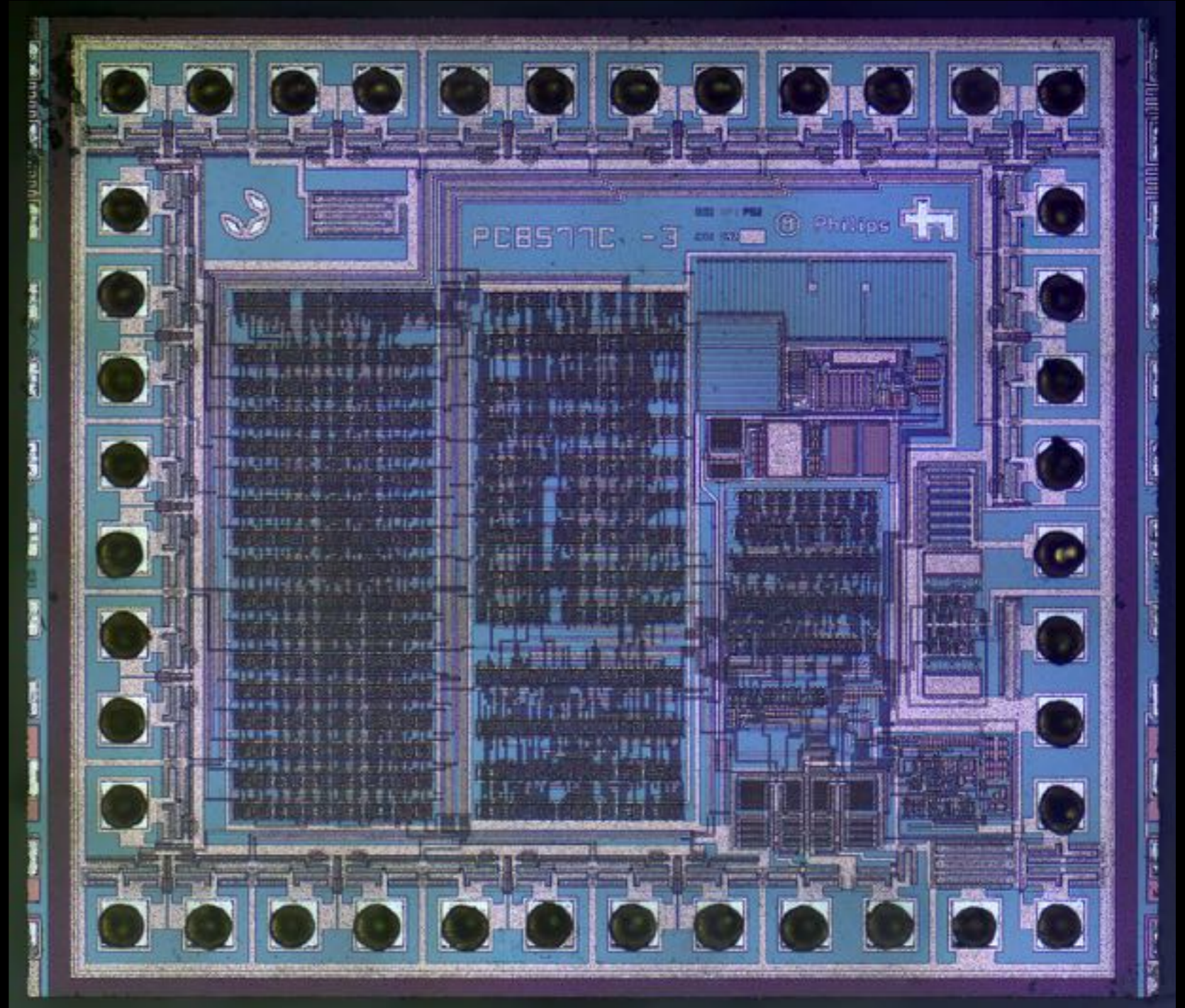- A microscope image of an integrated circuit used to control LCDs.
- Dark circles are the external connections to the IC.




Approach to topic

Integrated Circuit Design

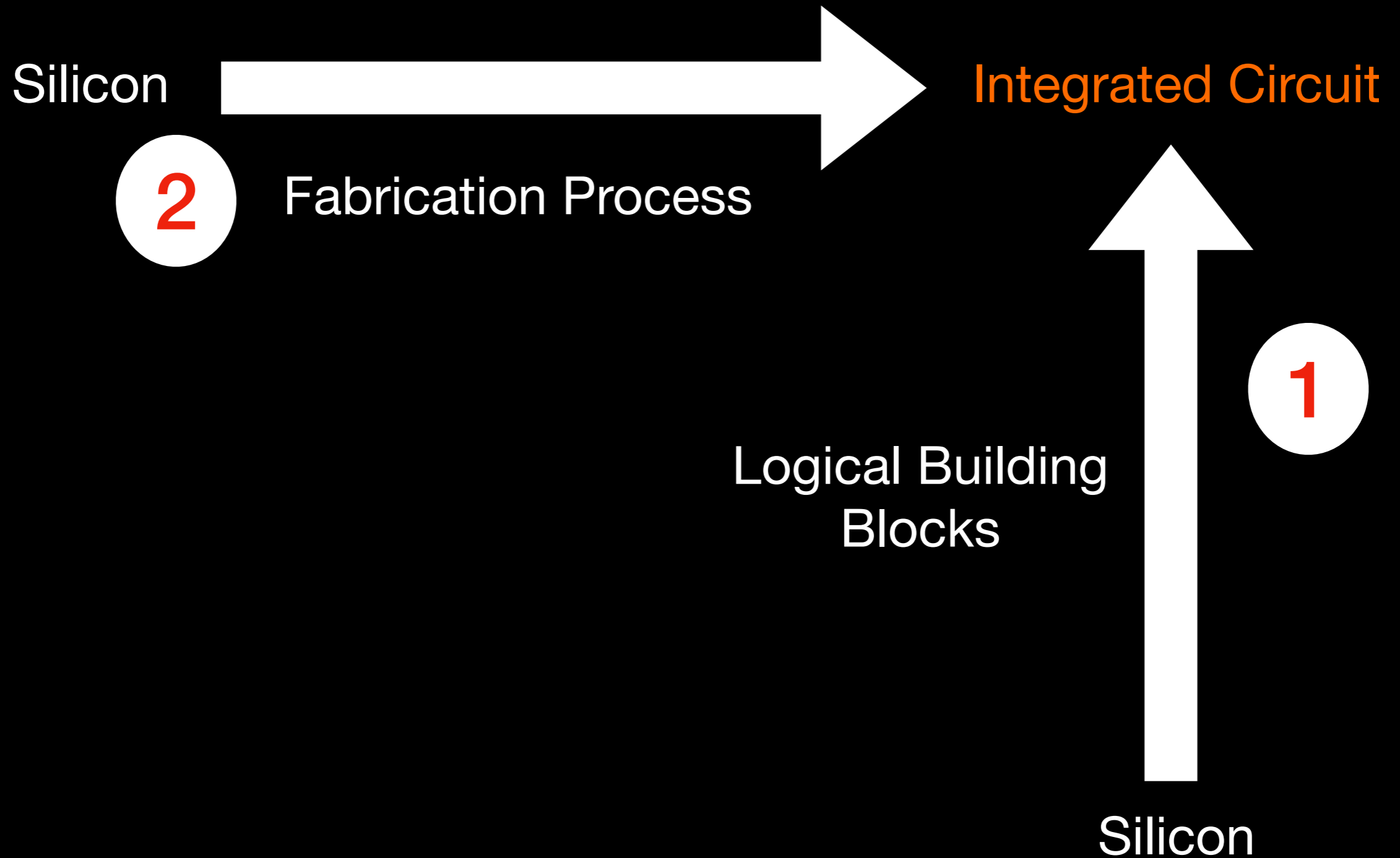


IC Building Blocks

Integrated Circuit Design

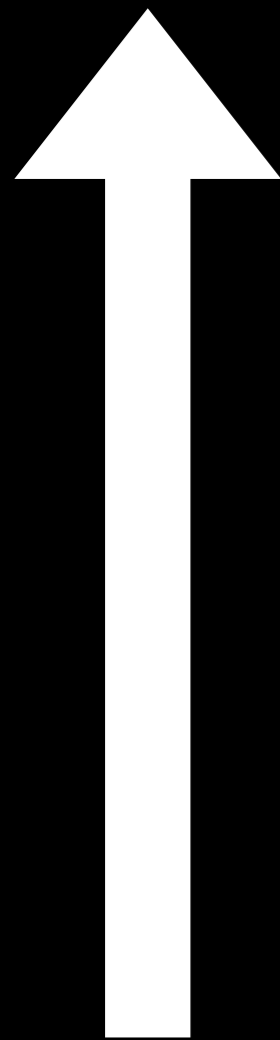


Integrated Digital systems	Microprocessor, Memory etc.
Digital system building blocks	adder, memory, flip-flop, shift register, counter...
Logic Gate Assemblies	AND, NAND, NOR, AOI (And Or Invert)...
Basic electronic components	Diode, transistor, capacitor, resistor
Silicon material	Pure wafer, semiconductor substrates


are made from

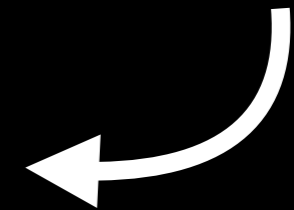


are made from

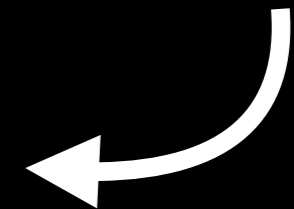

are made from

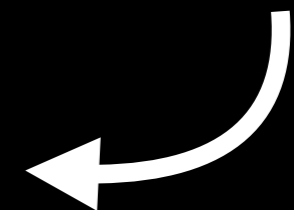

are made from

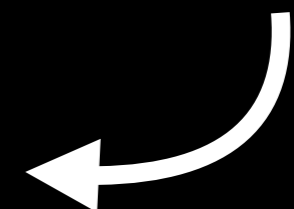

Semiconductor Material

Integrated Circuit Design

Silicon: the basic material - sand

Semiconductor material: Provides characteristics needed for electronic devices


The P-N Junction: The start point for diode & transistor technology

Silicon - the foundation material


Integrated Circuit Design



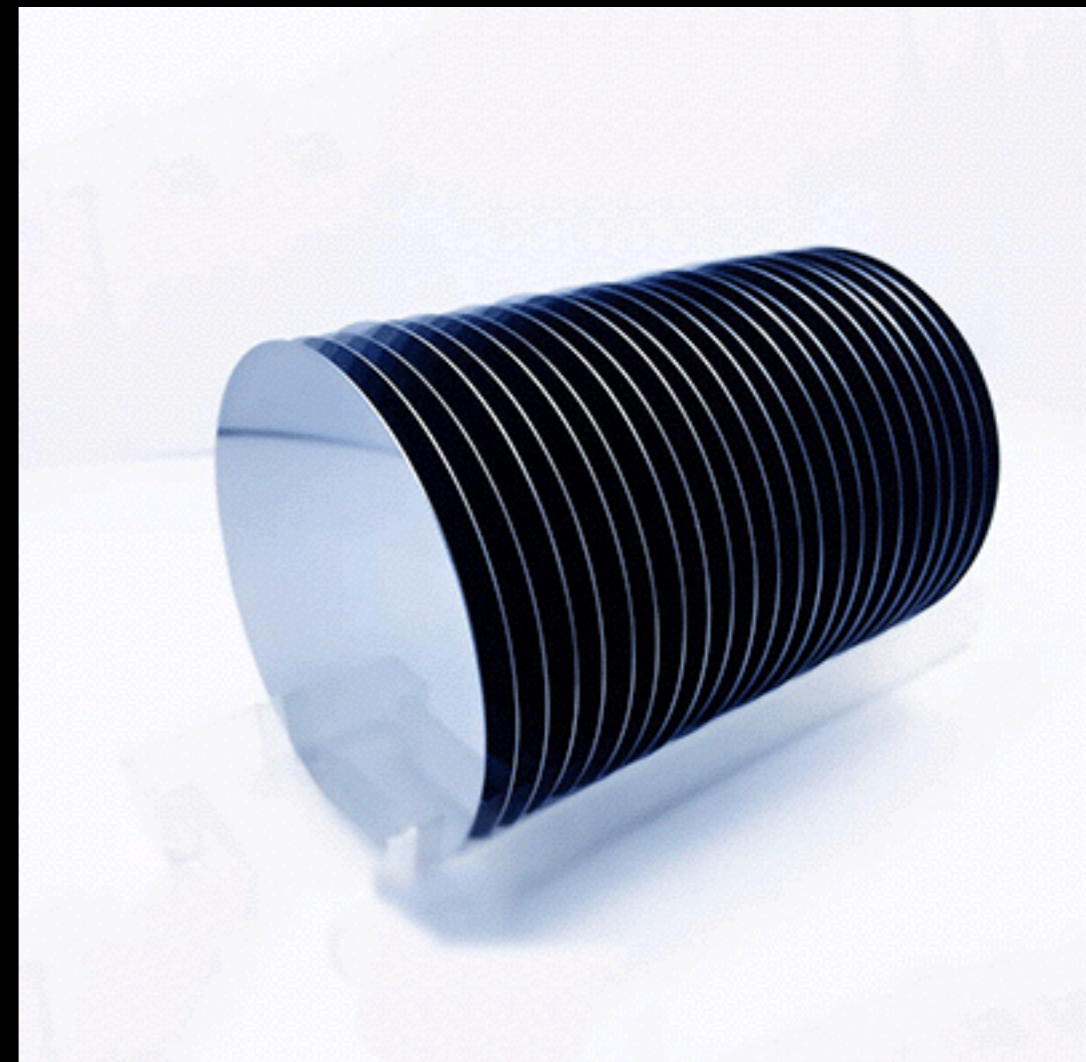IC production requires purification to better than 1 part per 10^{10} , and in special cases impurity levels below 1 part per 10^{12}





Models ease understanding

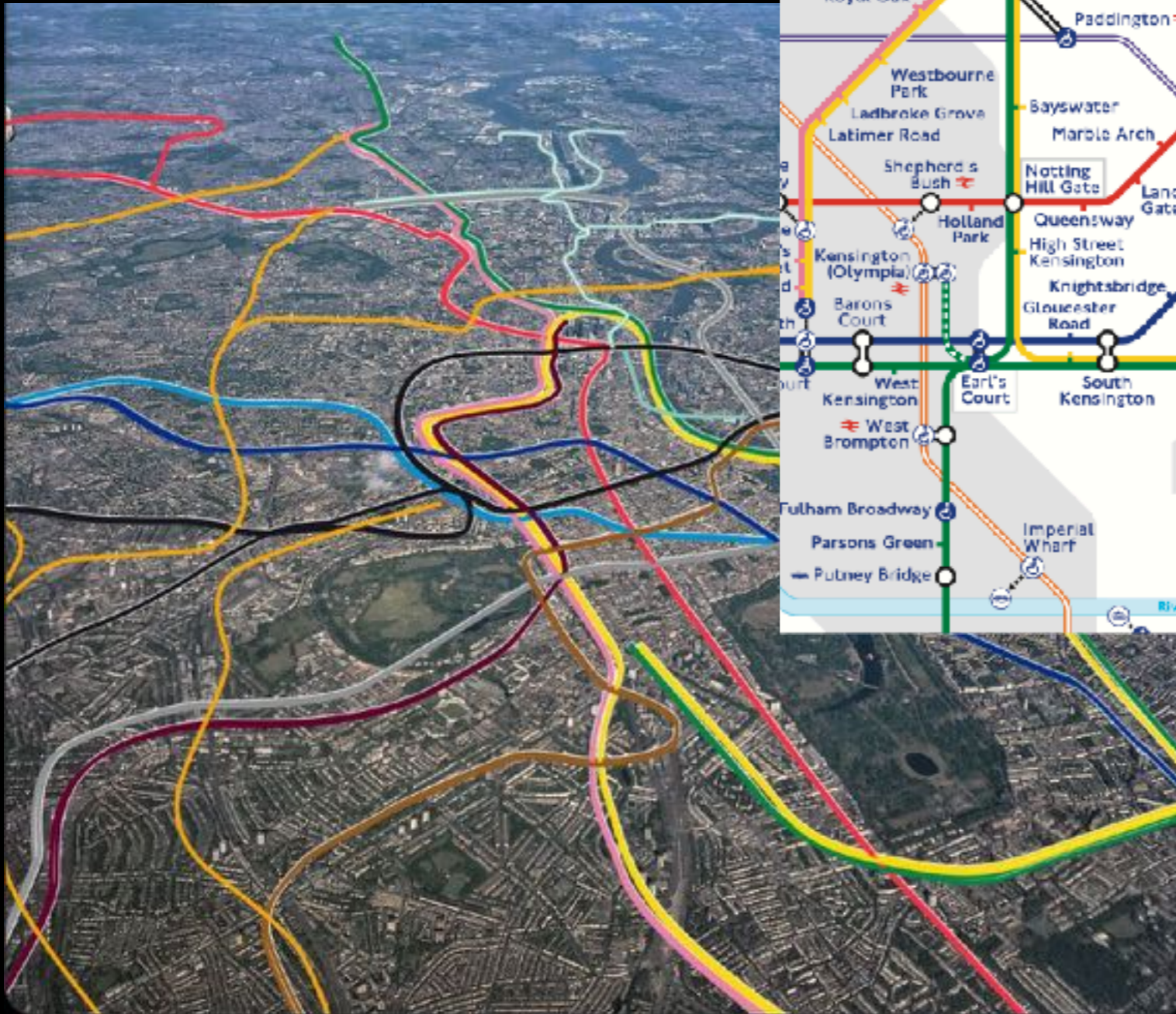


But are not truth

Silicon Atomic Structure

Integrated Circuit Design

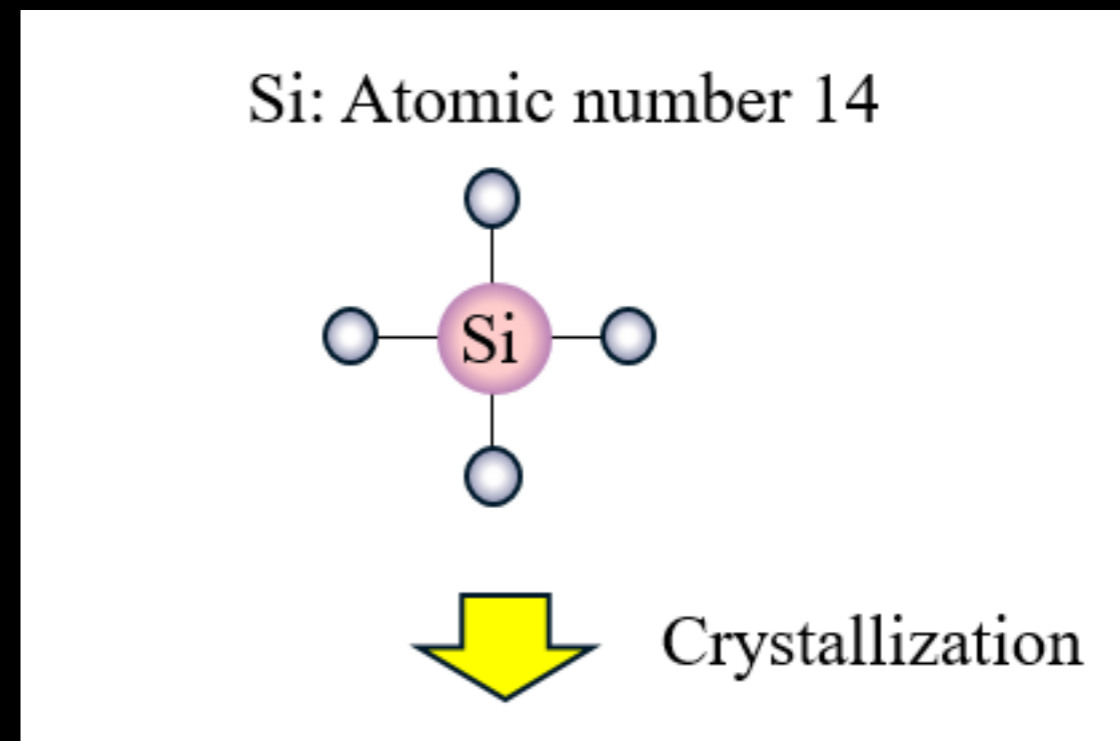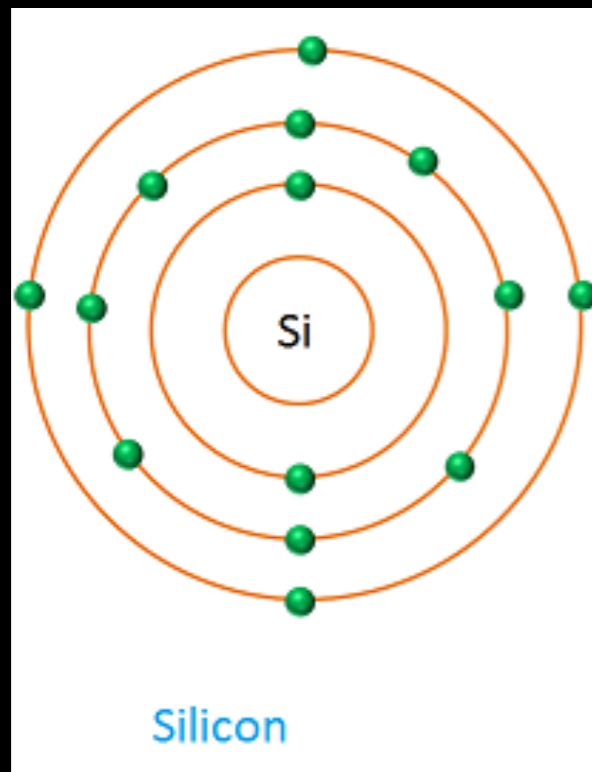

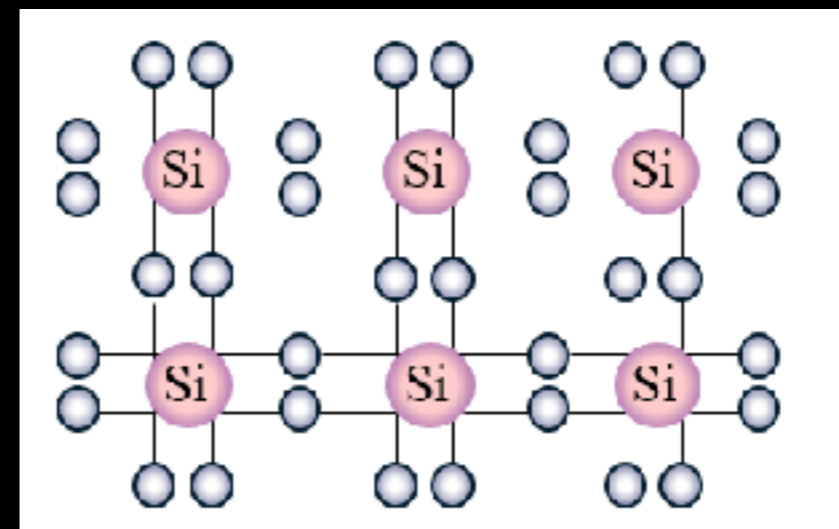
- Atoms have a “preferred” number of electrons in the outer ring
- Silicon have 4 electrons in the outer layer while 8 gives the most stable structure
- In crystal form, atoms “share” their outer electrons




Semiconductor Doping

Integrated Circuit Design

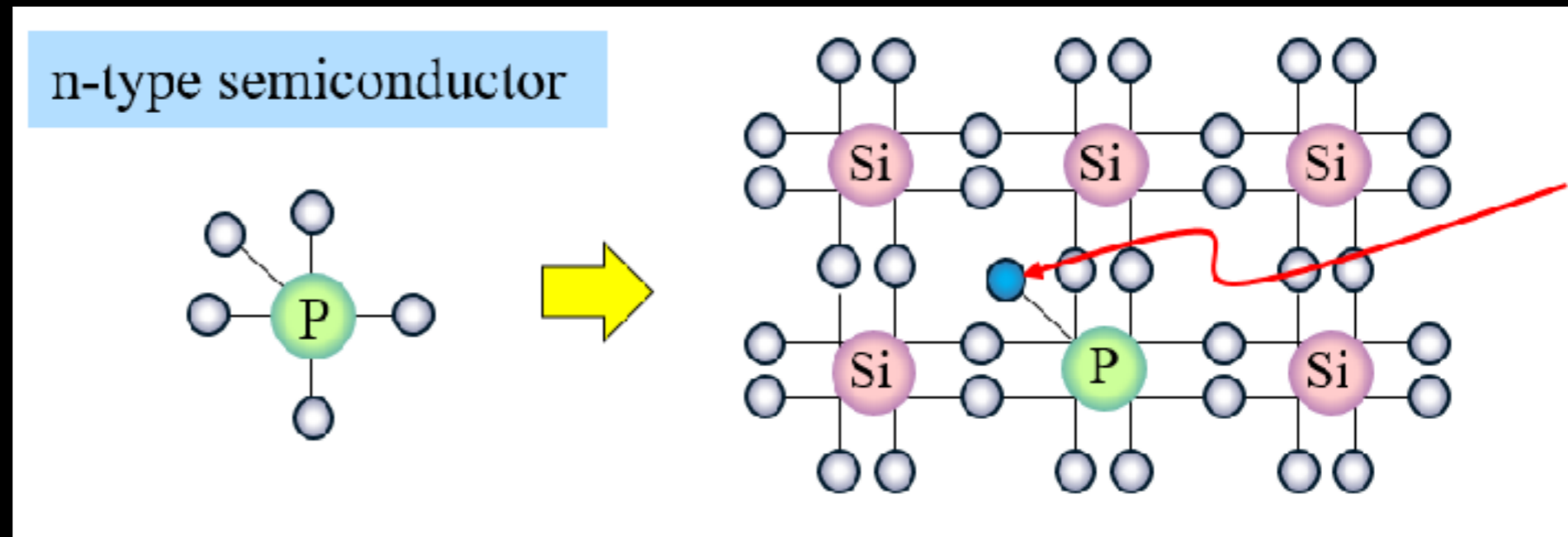- Phosphorus has 5 electrons in the outer layer
- Inserting Phosphorus atoms into the crystal structure gives rise to mobile electrons




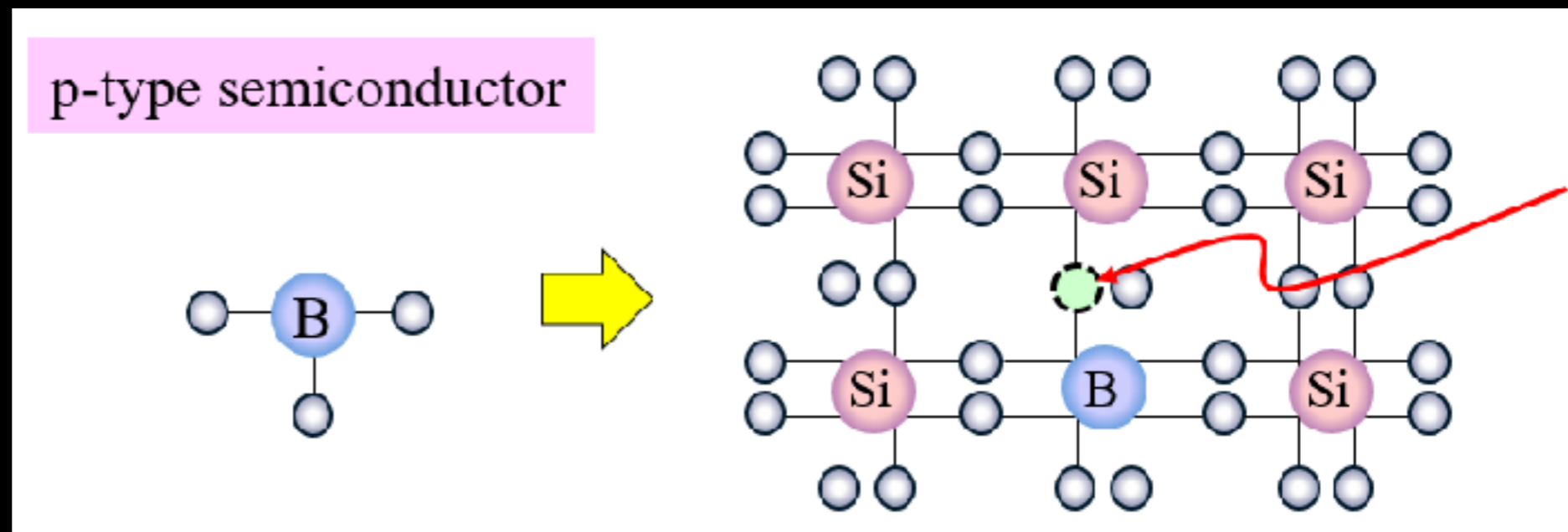- Boron has 3 electrons in the outer layer
- Inserting Boron atoms into the crystal structure gives rise to mobile "holes"




The P-N Junction


Integrated Circuit Design

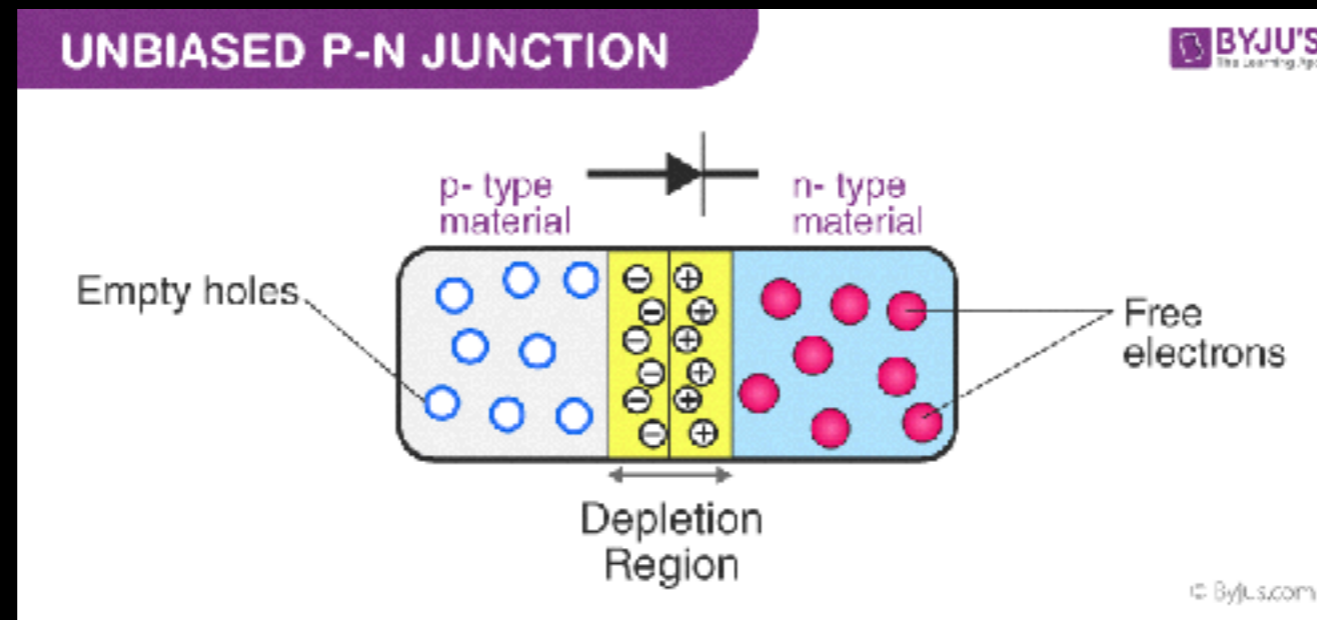

electron distribution - electric field

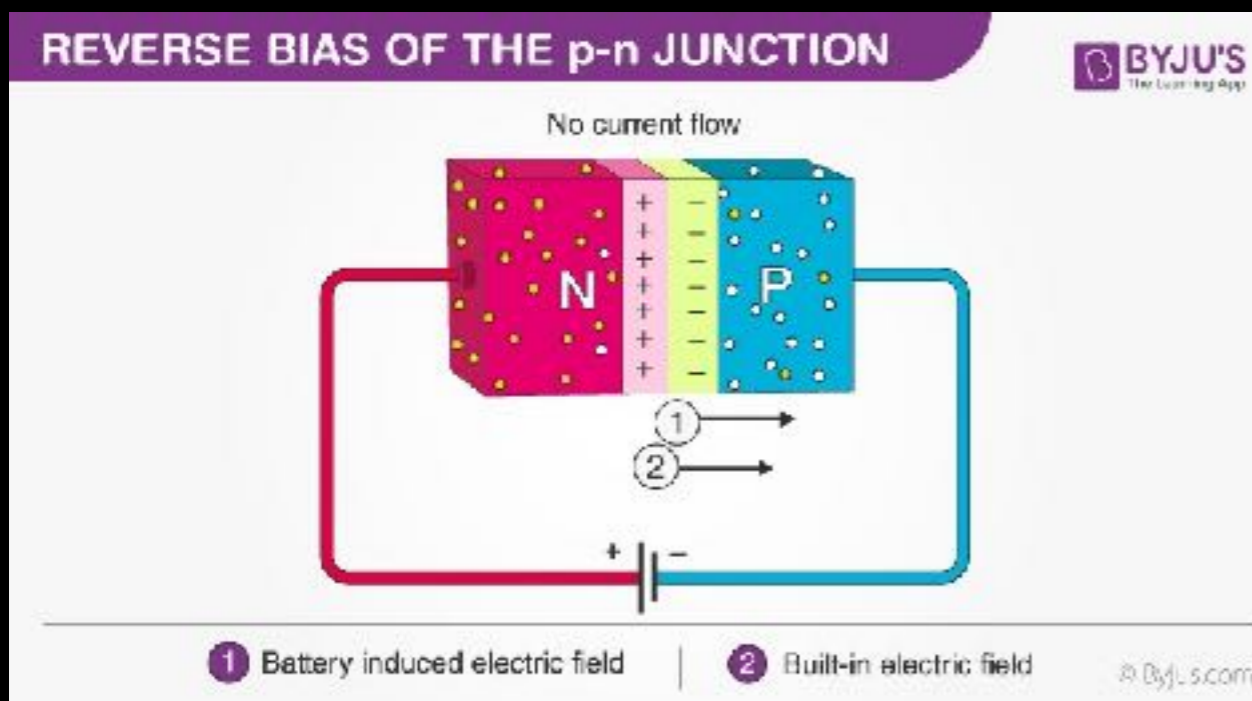

electric field stops current flow

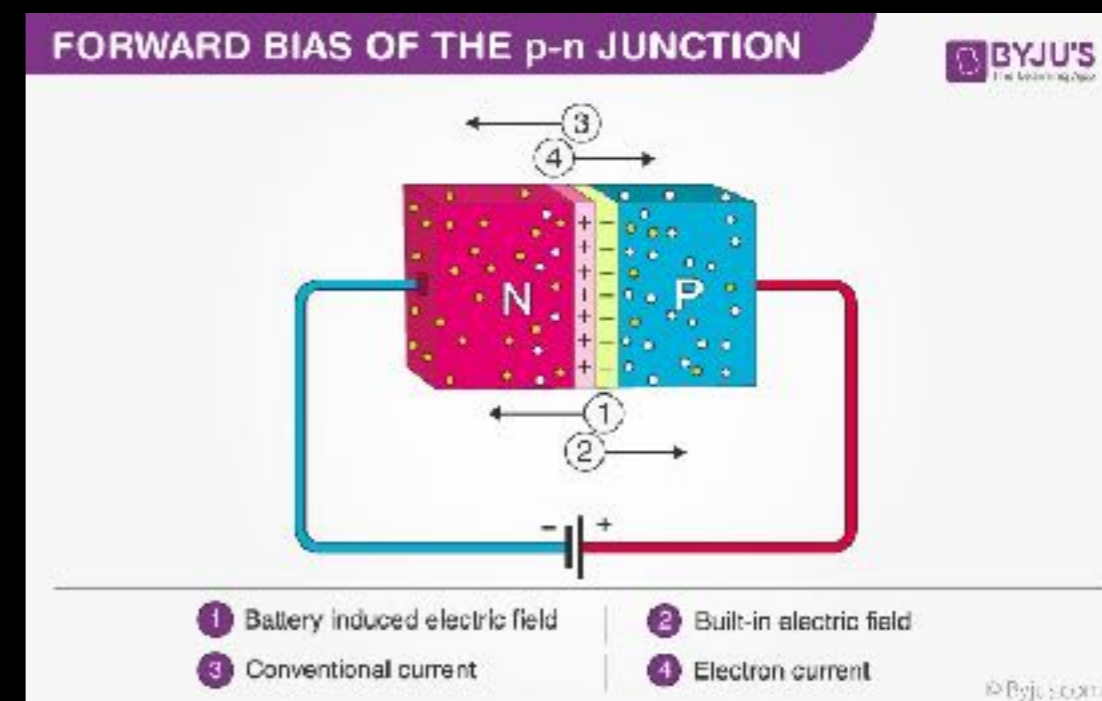

electric field allows current flow

Basic electronic components

Integrated Circuit Design



- Resistor:** A “drag” on electron flow. Causes voltage drop as electricity flows. (narrow pipe)
- Capacitor:** buffer, can store power (pipe with rubber membrane)
- Diode:** One way only transmission (one way valve)
- Transistor:** voltage operated valve - turns on and off the flow of electricity. (tap)

Transistor

Integrated Circuit Design

MOSFET Transistor
(Metal Oxide Semiconductor
Field Effect Transistor)

Used as a switch

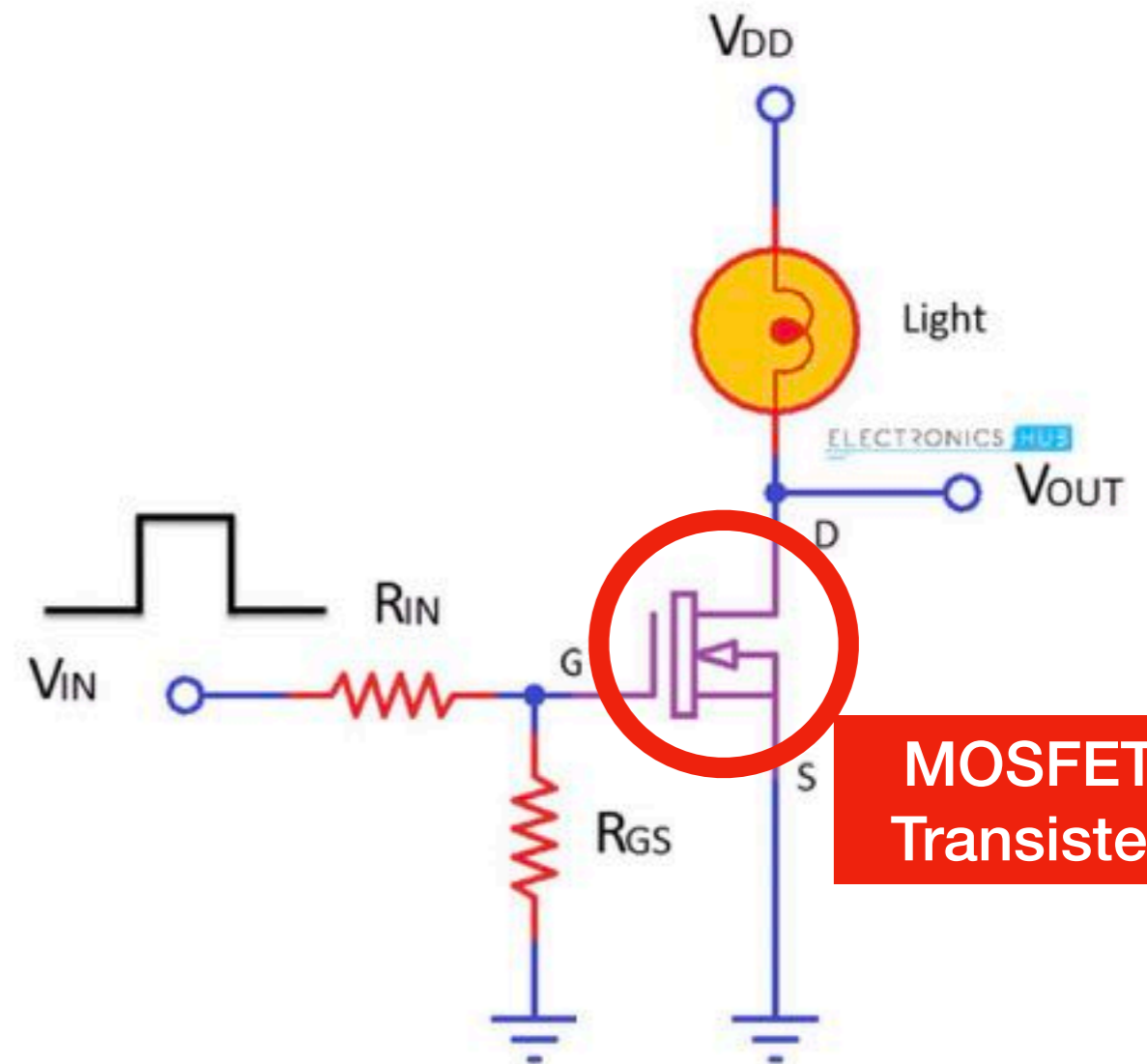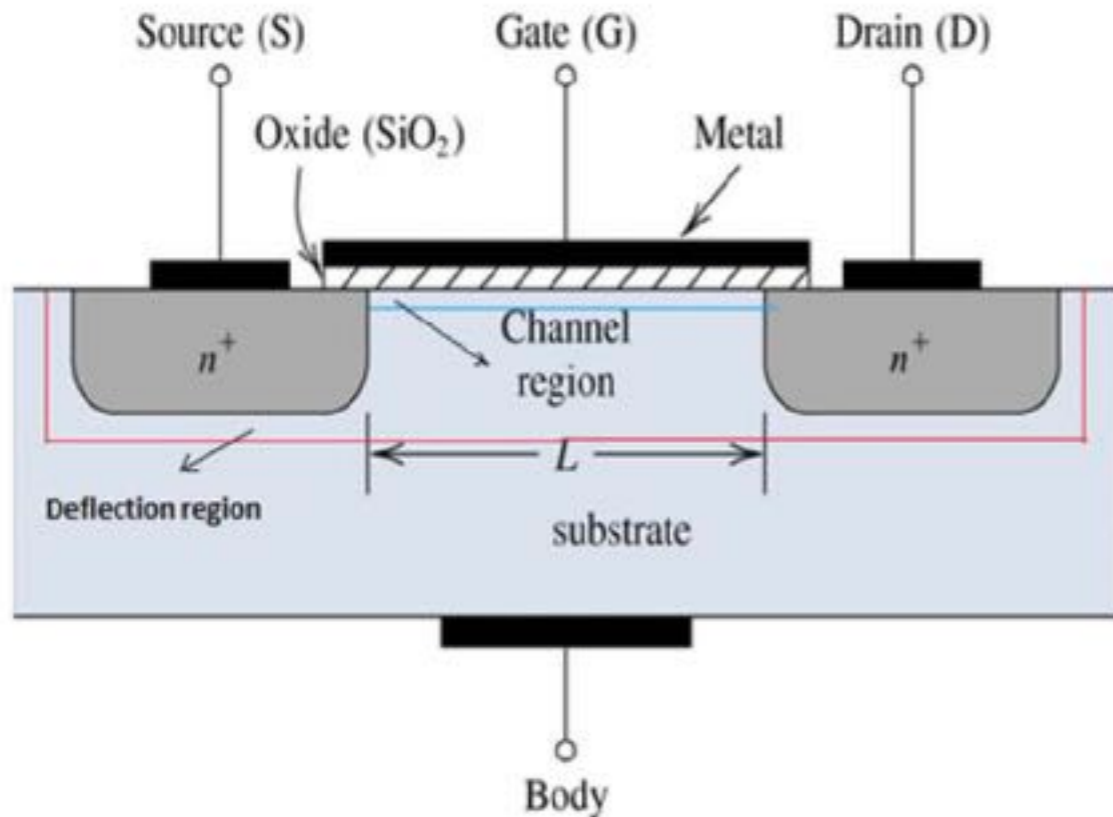

Logic Gates

Integrated Circuit Design

AND


NAND = Not AND

NOR = Not OR

XOR = Exclusive OR

AOI = AND or INVERT

AND

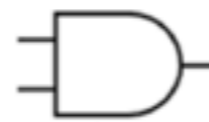

INPUT		OUTPUT
A	B	
0	0	0
1	0	0
0	1	0
1	1	1

OR



INPUT		OUTPUT
A	B	
0	0	0
1	0	1
0	1	1
1	1	1

XOR



INPUT		OUTPUT
A	B	
0	0	0
1	0	1
0	1	1
1	1	0

NAND



INPUT		OUTPUT
A	B	
0	0	1
1	0	1
0	1	1
1	1	0

NOR



INPUT		OUTPUT
A	B	
0	0	1
1	0	0
0	1	0
1	1	0

XNOR




INPUT		OUTPUT
A	B	
0	0	1
1	0	0
0	1	0
1	1	1

Logic Gates (AND, NAND, NOR, AOI)

Integrated Circuit Design


NAND symbol &
logic table

NAND gate

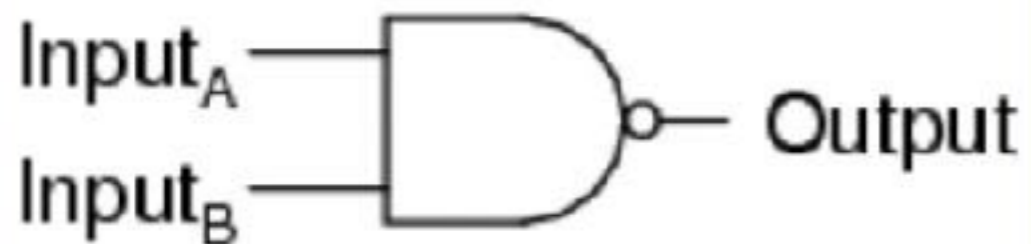

A	B	Output
0	0	1
0	1	1
1	0	1
1	1	0

NAND circuit

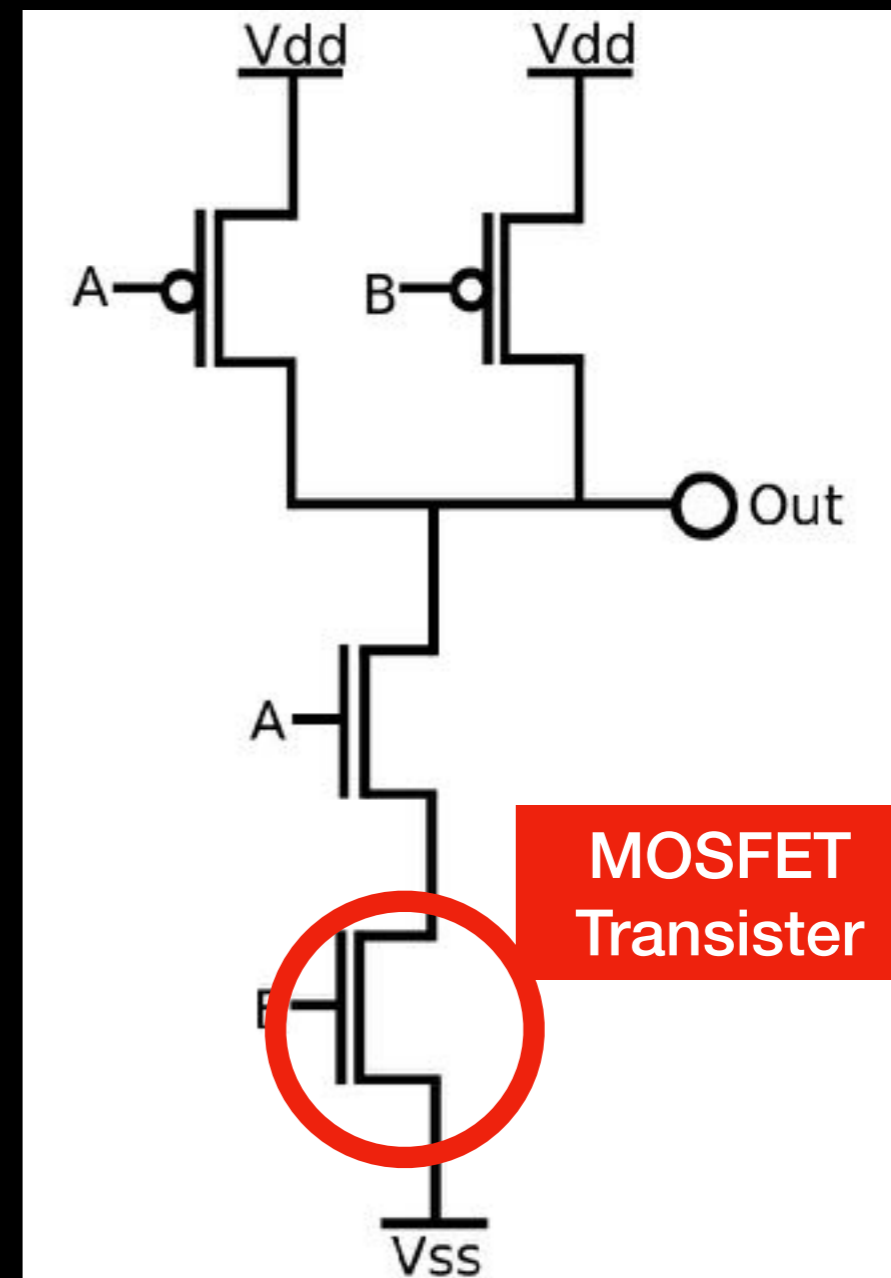

Digital System building blocks

Integrated Circuit Design

adder:	Sums binary numbers
memory:	Stores binary number
flip-flop:	typically toggle output on pulse
shift register:	typically used to convert serial to parallel data
counter:	typically input clock pulses & output count

Full adder (carry in / carry out)

Integrated Circuit Design


Binary

Decimal number	Binary number
0	0
1	1
2	10
3	11
4	100
5	101
6	110
7	111
8	1000
9	1001
10	1010
11	1011
12	1100
13	1101
14	1110
15	1111


Adder truth table (C = Carry)

Inputs			Outputs	
A	B	C _{in}	C _{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

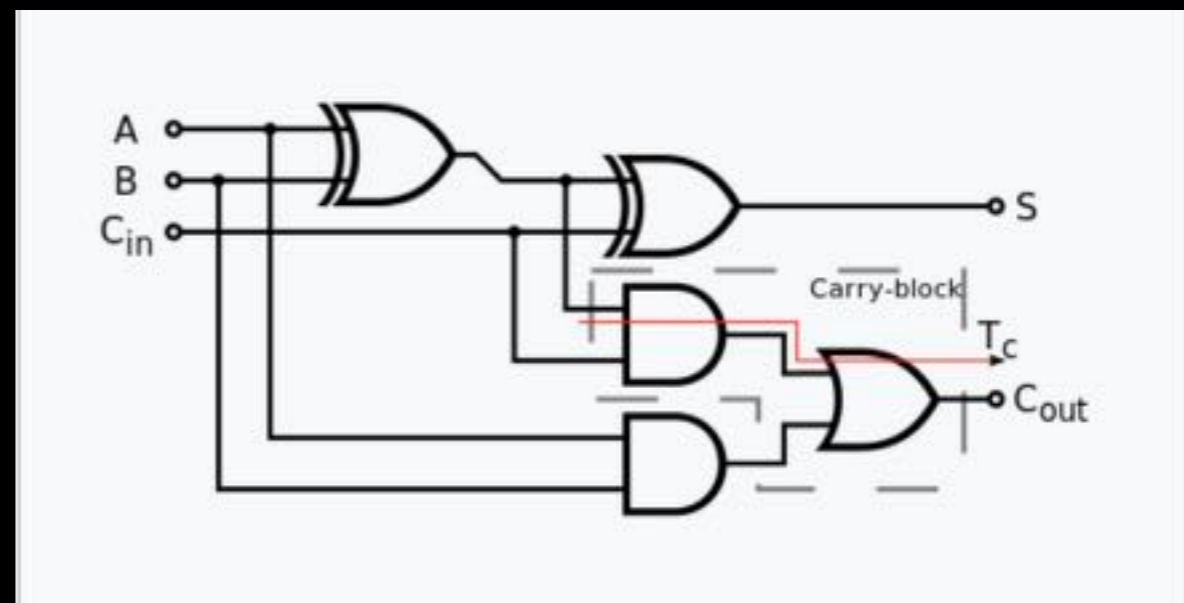1 bit Full Adder Logic
2 XOR gates, 2 AND gates, 1 OR gate.




4 bit adder

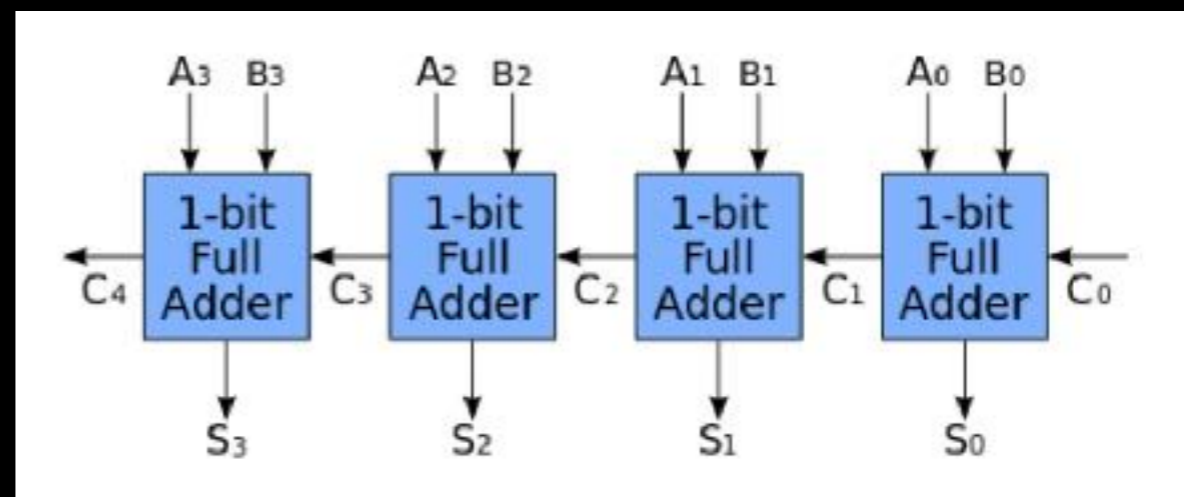


ARM Processor Architecture

Integrated Circuit Design

ARM Integrated Circuit

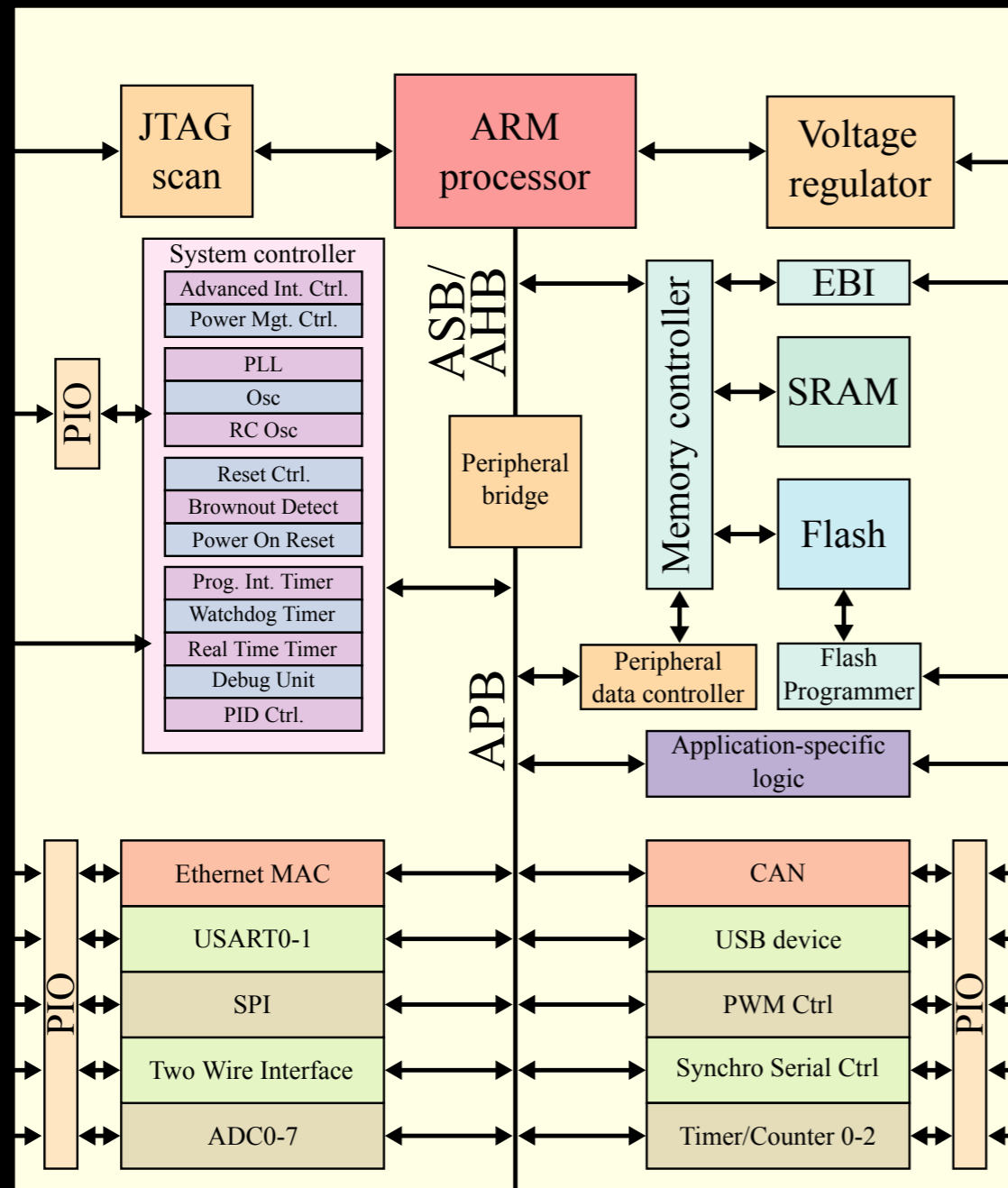


ARM processor

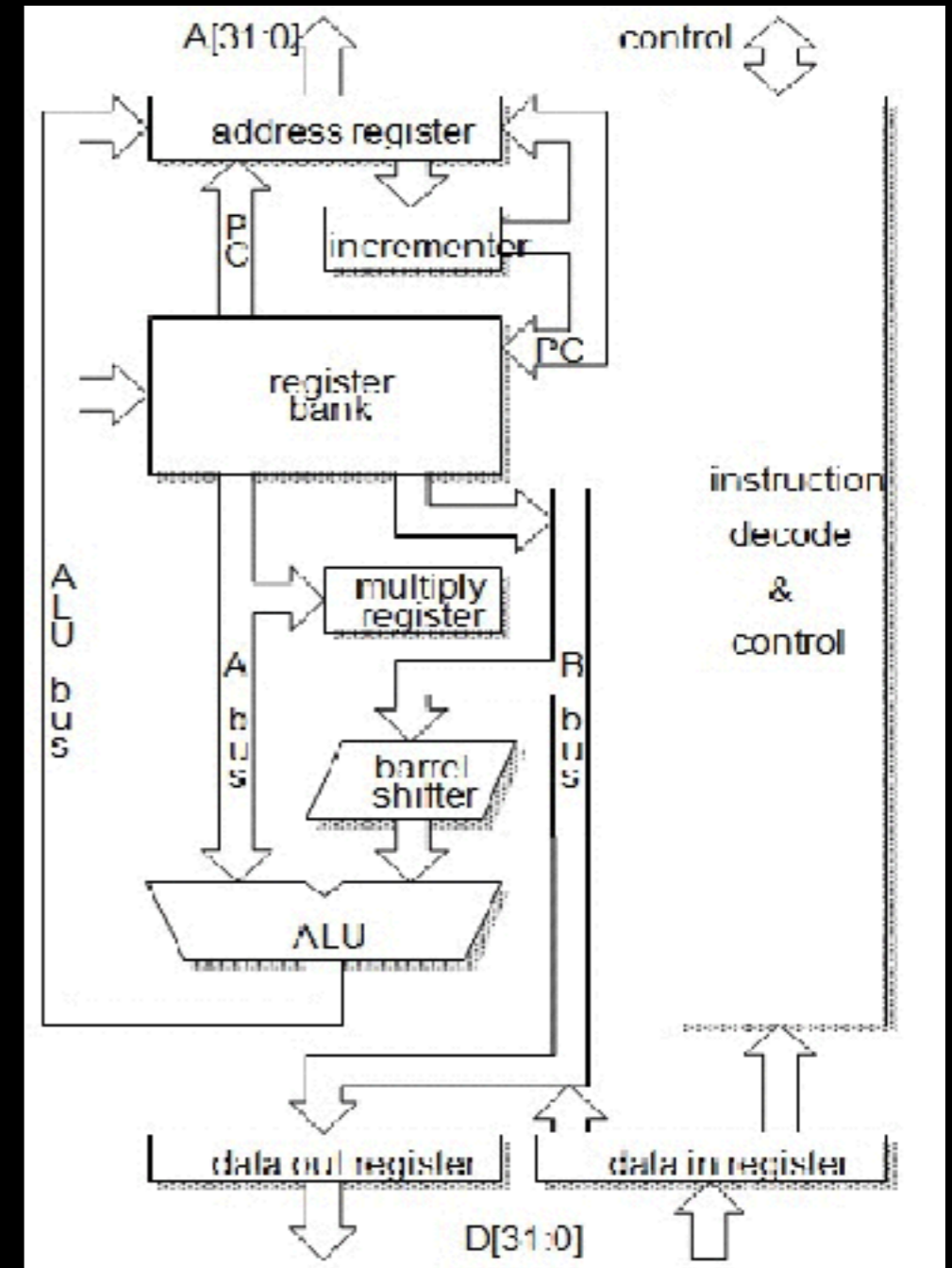

ARM Processor


Integrated Circuit Design

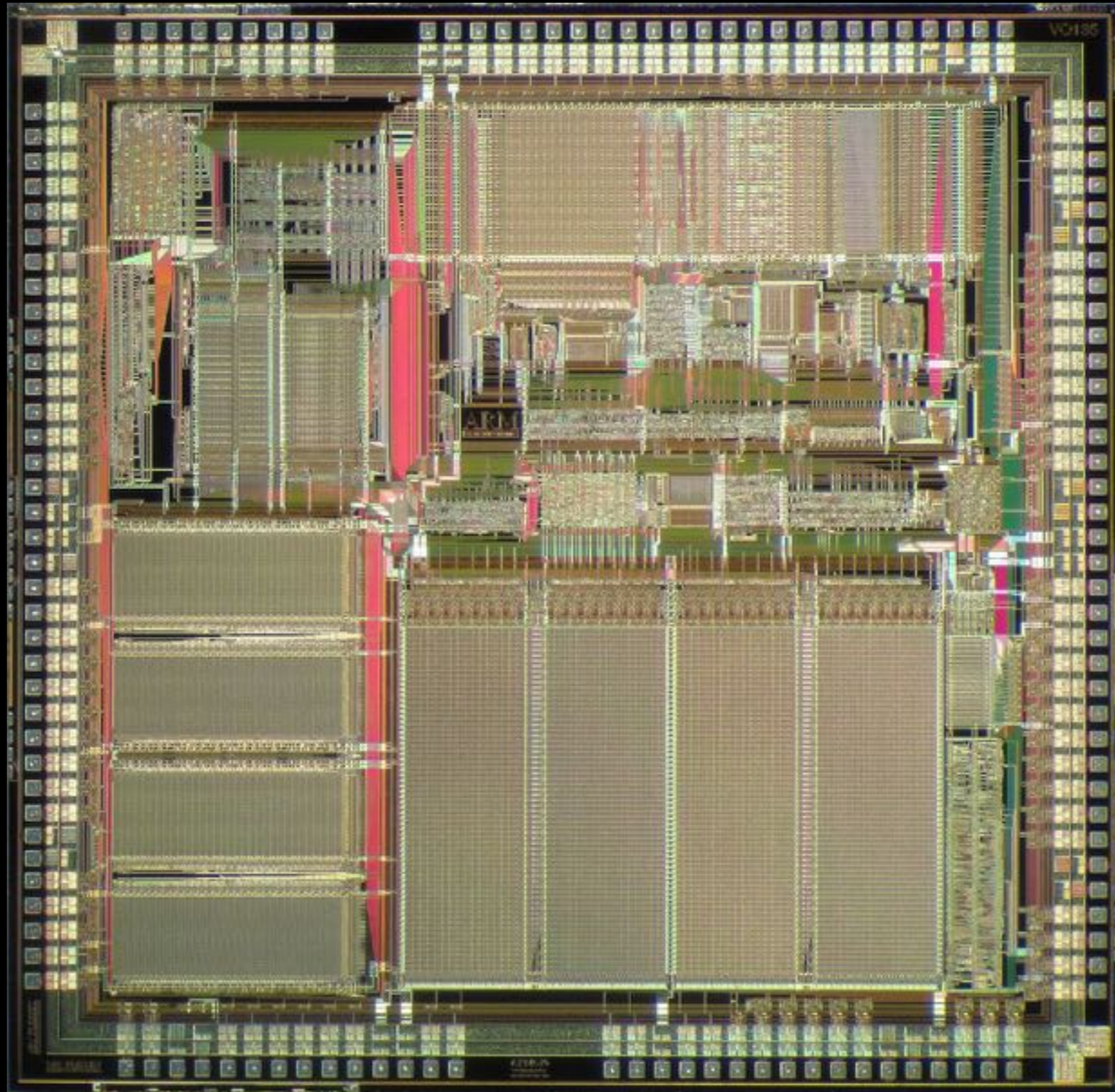

Fabrication Process

Integrated Circuit Design

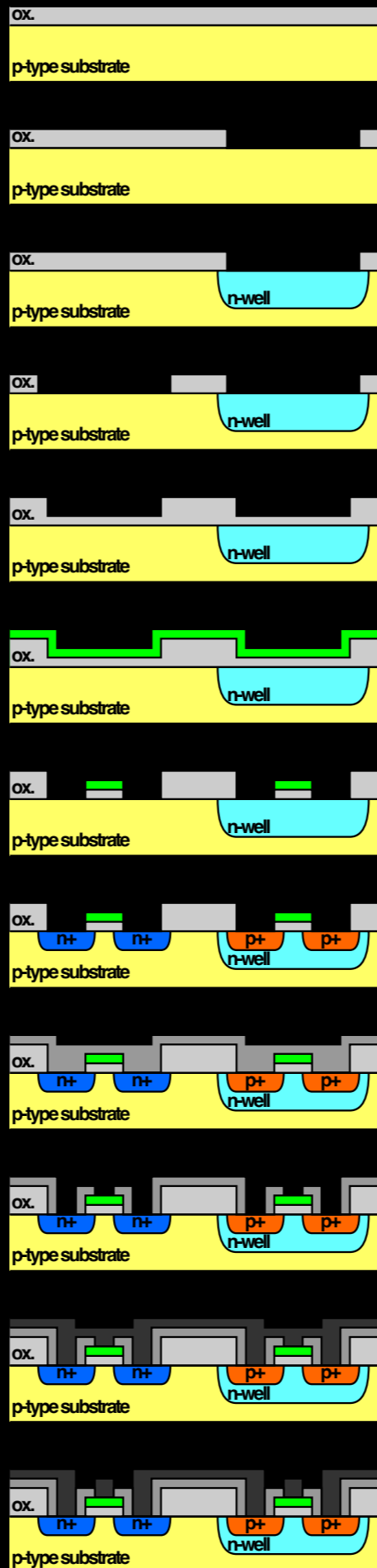Simplified process of fabrication of a CMOS inverter on p-type substrate in semiconductor micro fabrication.



1. Grow field oxide
2. Etch oxide for pMOSFET
3. Diffuse n-well
4. Etch oxide for nMOSFET
5. Grow gate oxide
6. Deposit polysilicon
7. Etch polysilicon and oxide
8. Implant sources and drains
9. Grow nitride
10. Etch nitride
11. Deposit metal
12. Etch metal

Video shown in Meeting

Integrated Circuit Design

- <https://www.computerhistory.org/revolution/digital-logic/12/288/2220>
-

Questions?